

---


# Lab. 9

## Frequency Response of Transistors



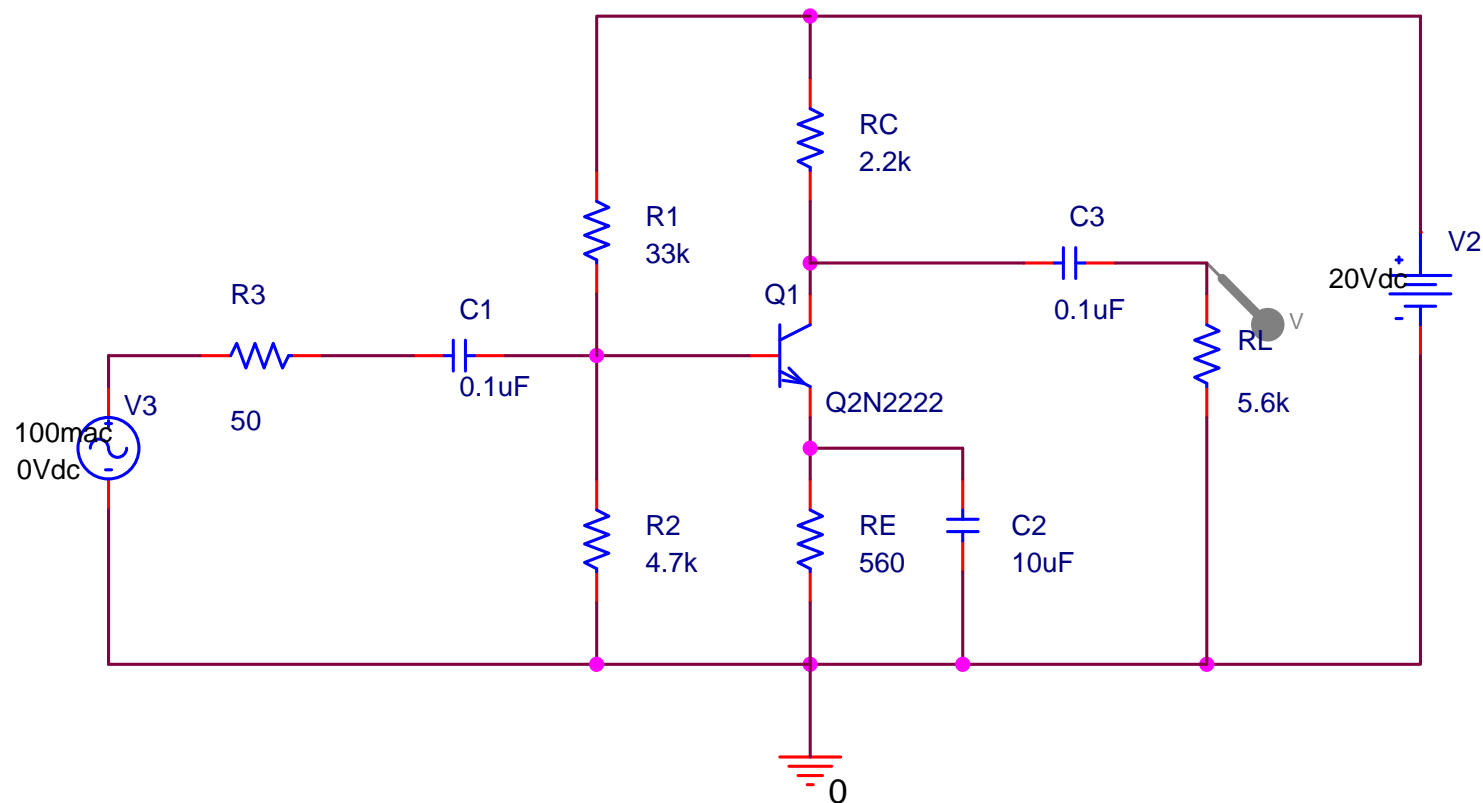
# Transistor Frequency Response

- ✓ Test circuit for TR frequency response (pp. 306, Fig. 17-15)


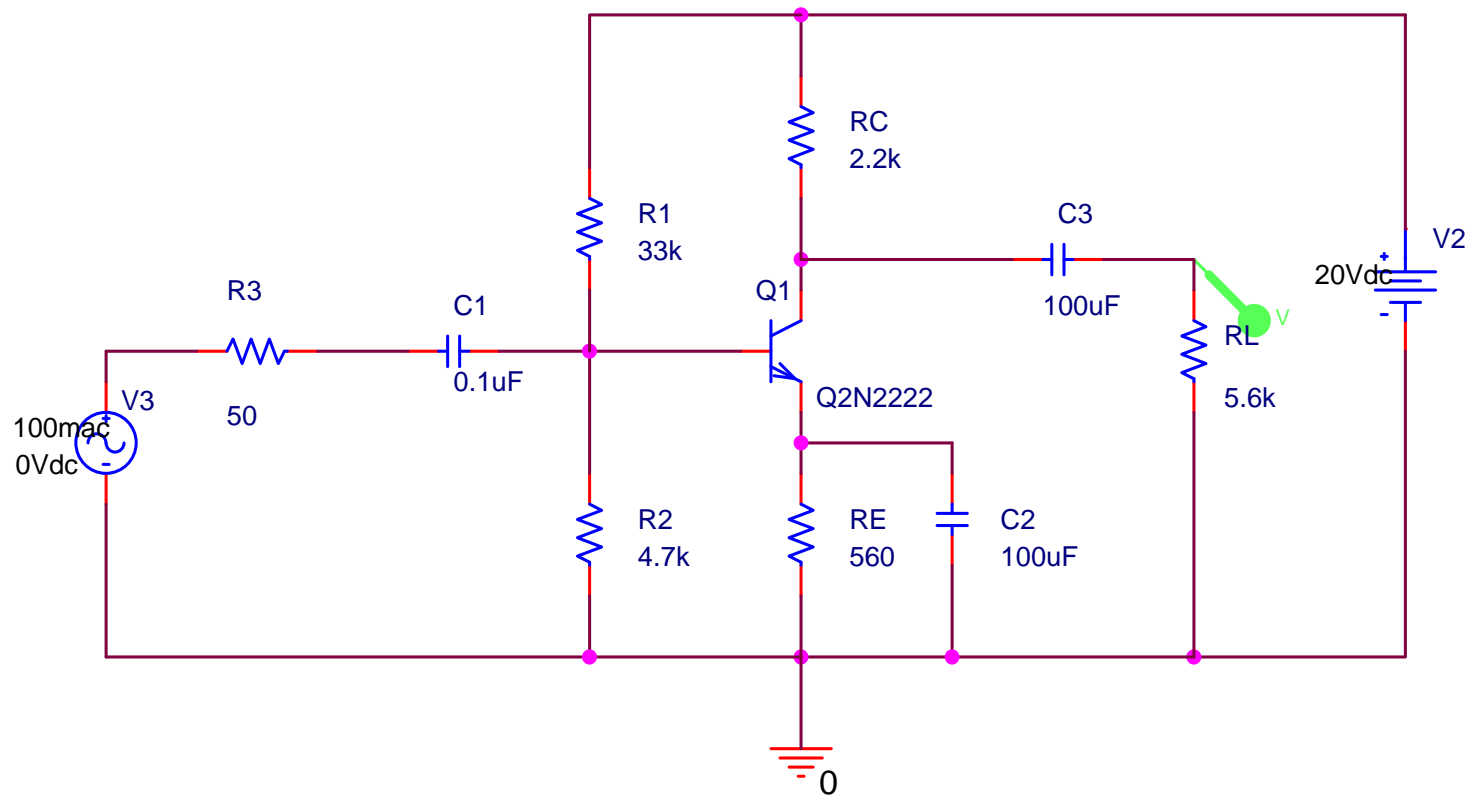
# Transistor Frequency Response

- ✓ TR frequency response (pp. 306, Fig. 17-15,  $C = 100\mu\text{F}$ )



# Contents of Lab. Report

---

- ✓ Team No.:                      PID:                      Name:
- ✓ Introduction
- ✓ Test Results of Transistor Frequency Responses
- ✓ Discussion & Conclusion



# Pre-Report (Lab. 10)

---

- ✓ PSPICE simulations of a power amplifier circuit!
- ✓ Submit the schematic diagrams and the simulation results.
- ✓ No need of introduction and discussion in pre-report.

