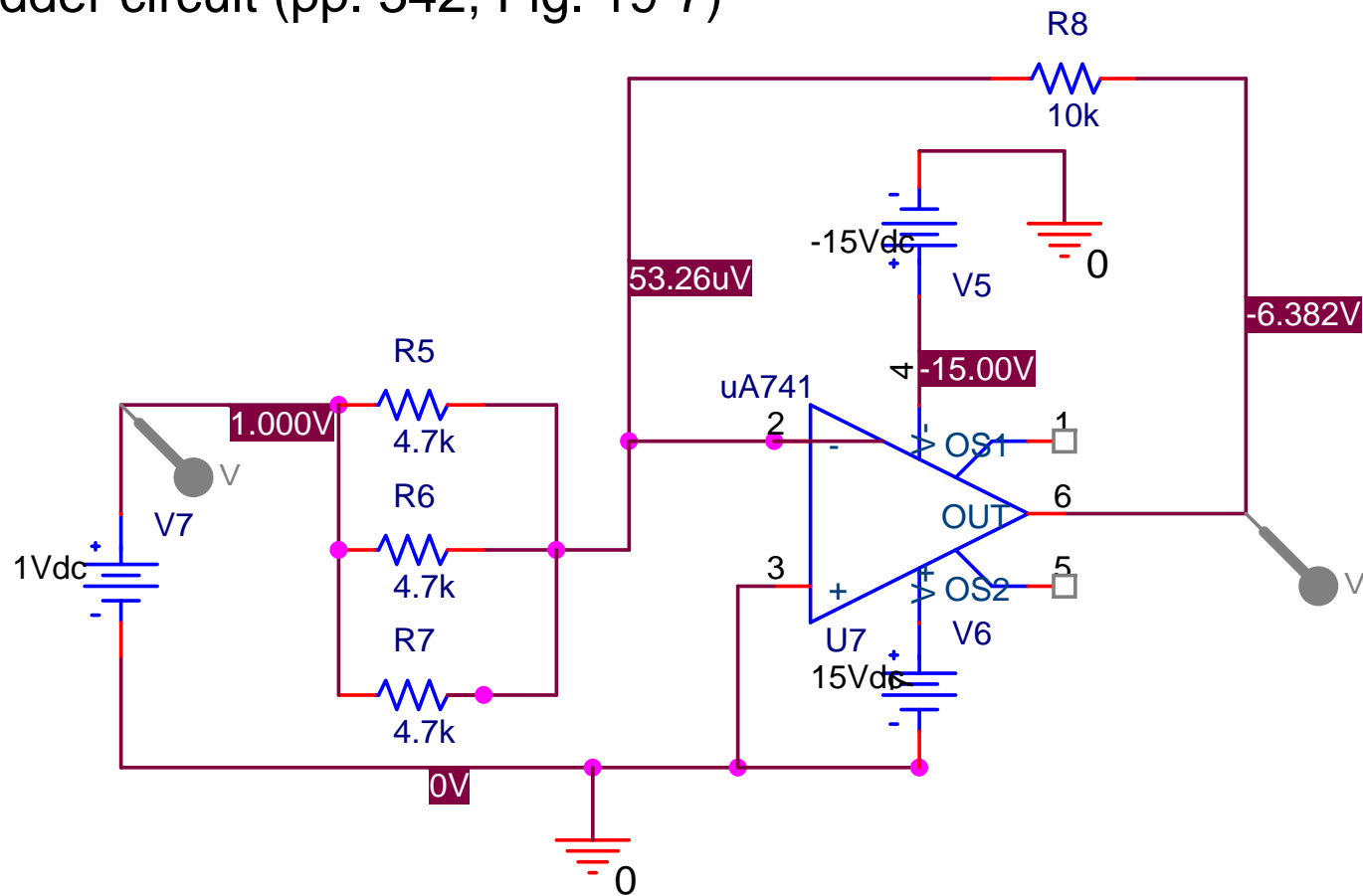

Lab. 12

Operational Amplifiers #2




Adder

- ✓ Adder circuit (pp. 342, Fig. 19-7)




Differentiator

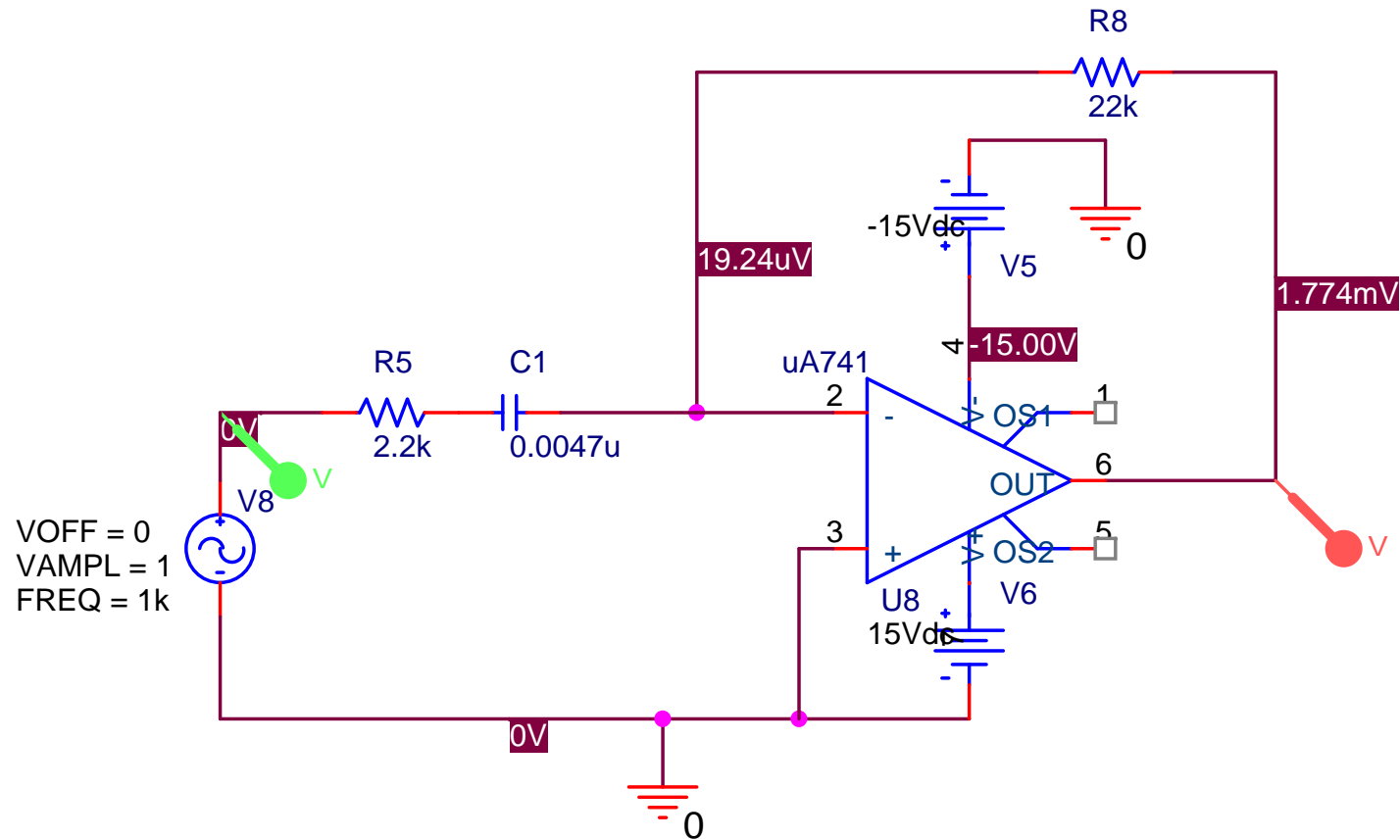- ✓ Differentiator circuit (pp. 343, Fig. 19-8)



Integrator

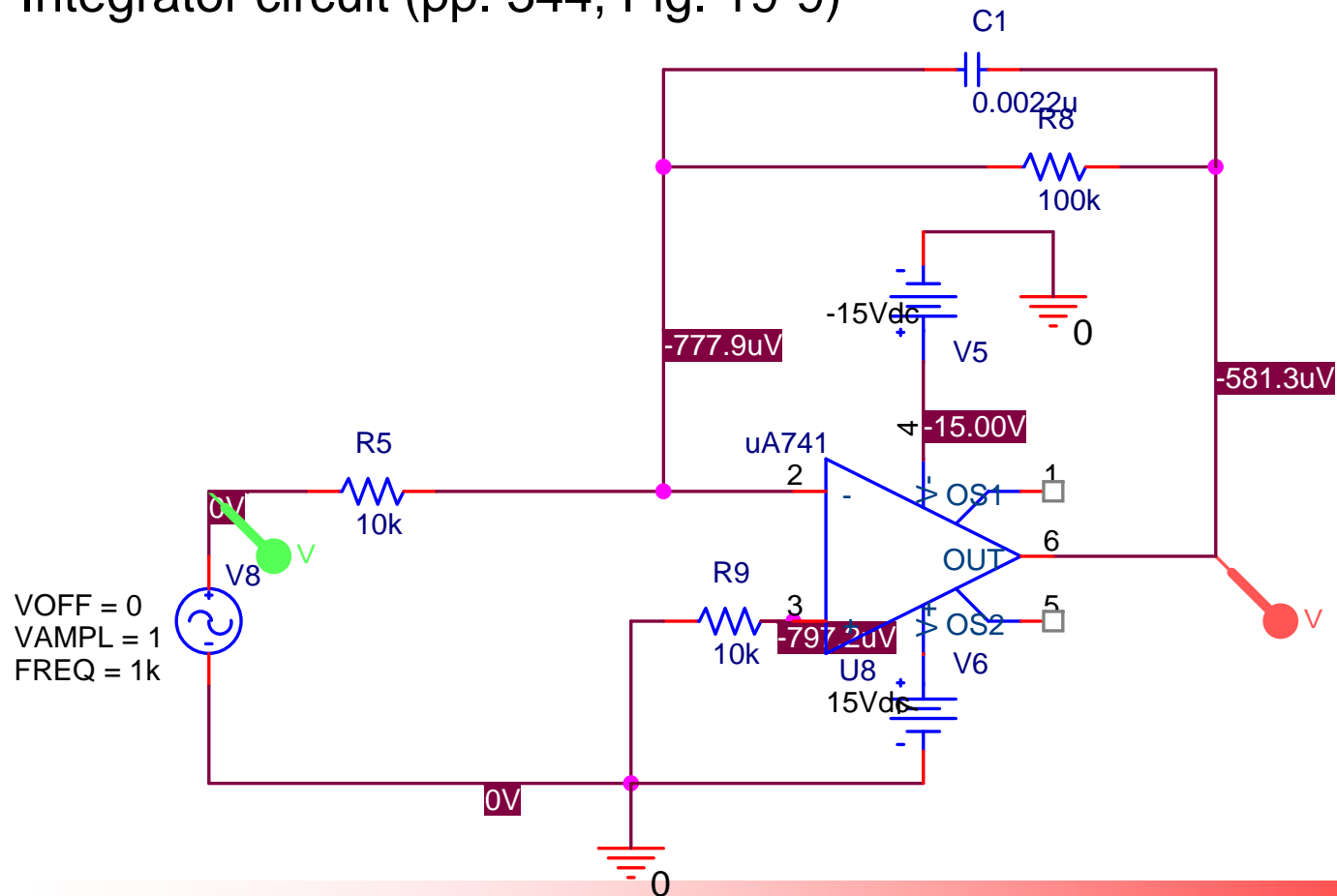- ✓ Integrator circuit (pp. 344, Fig. 19-9)



Contents of Lab. Report

- ✓ Team No.: _____ PID: _____ Name: _____
- ✓ Introduction
- ✓ Test Results: adder, differentiator, integrator
- ✓ Discussion & Conclusion

