



# CHAPTER 1

## PSPICE simulations & Bias circuits for voltage divider




# Devices on evaluation board

---

- ✓ Diode: D1N4148
- ✓ Zener diode: D1N750
- ✓ BJT: Q2N2222(npn), Q2N3906(pnp)
- ✓ MOSFET: IRF150(Enhancement-mode N-channel)
- ✓ OP-AMP: uA741


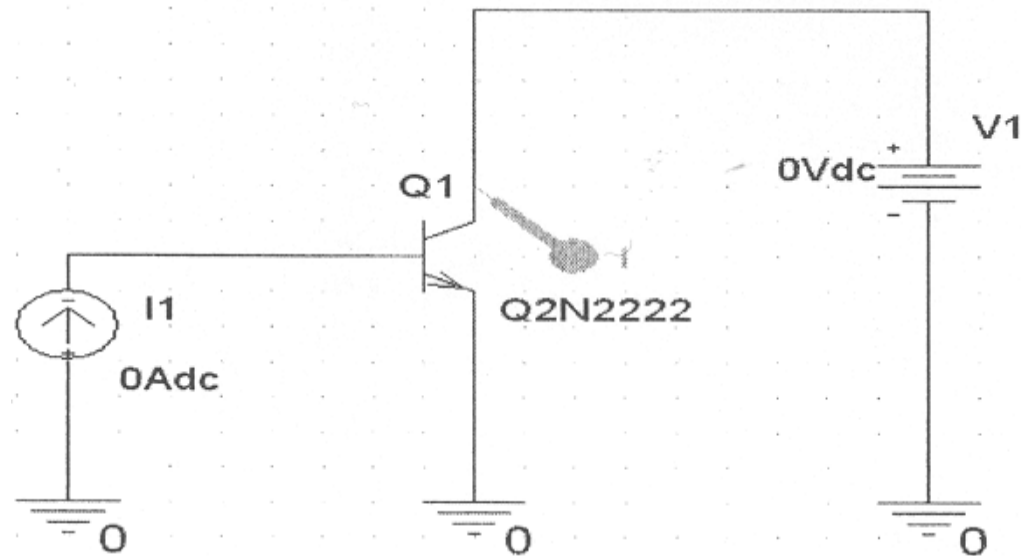
# $V_{CE} - I_C$ Characteristic Simulations




Common-Emitter Circuit for V-I Simulations




# $V_{CE} - I_C$ Characteristic Simulations

- DC sweep

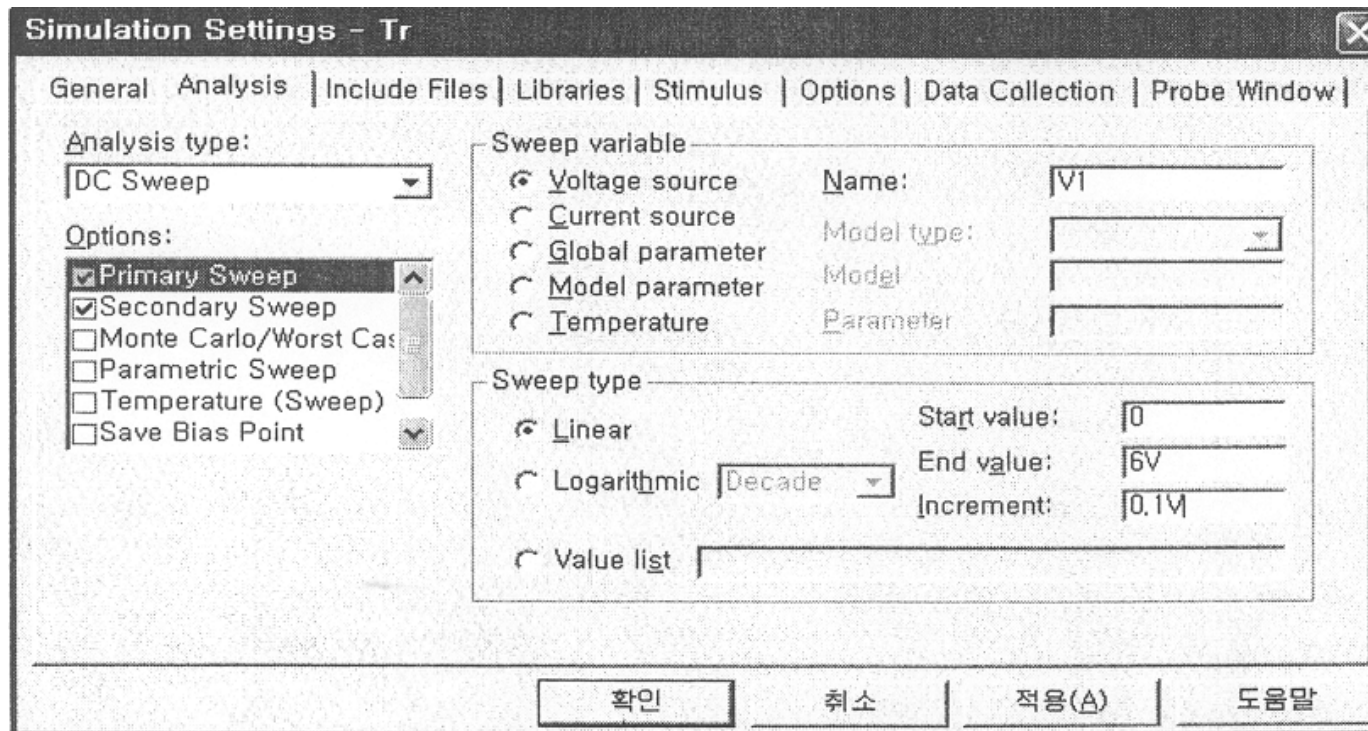

# $V_{CE} - I_C$ Characteristic Simulations


- Secondary sweep

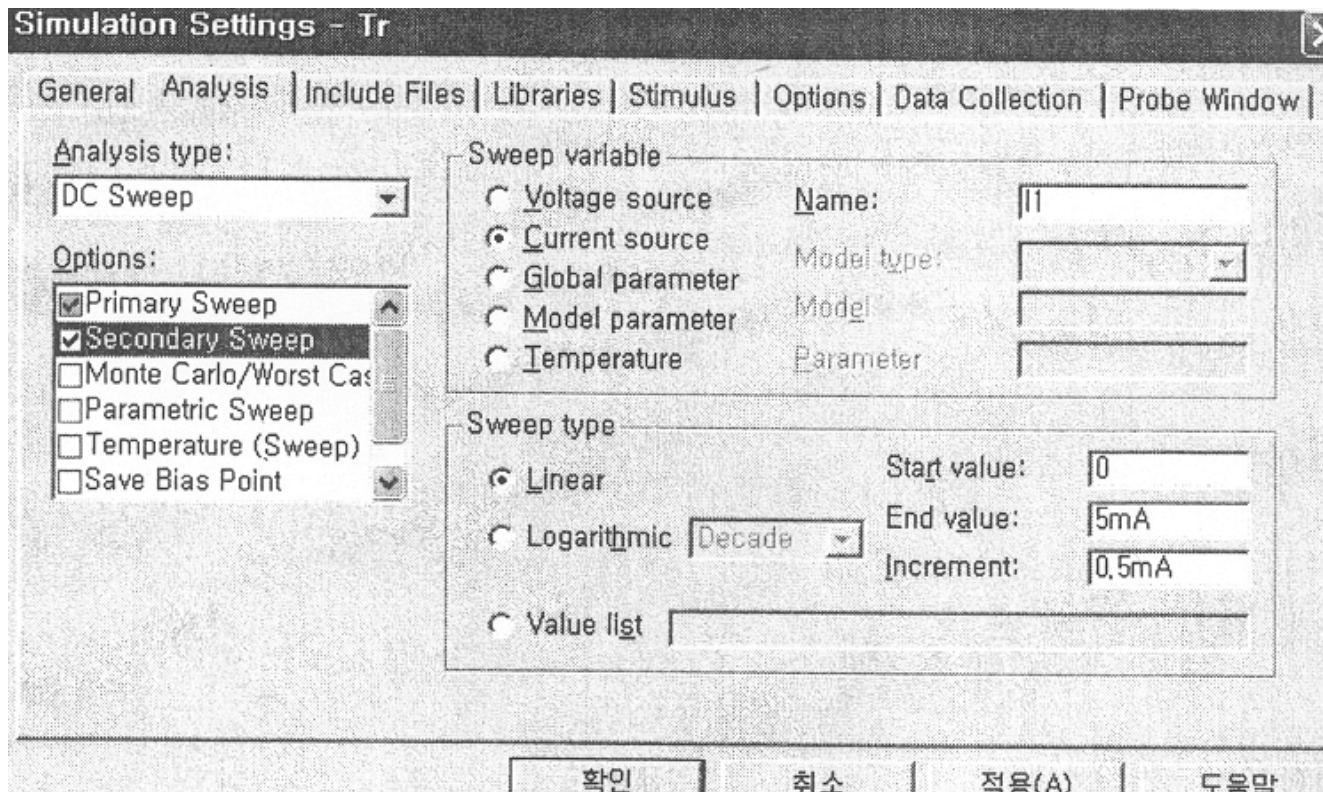



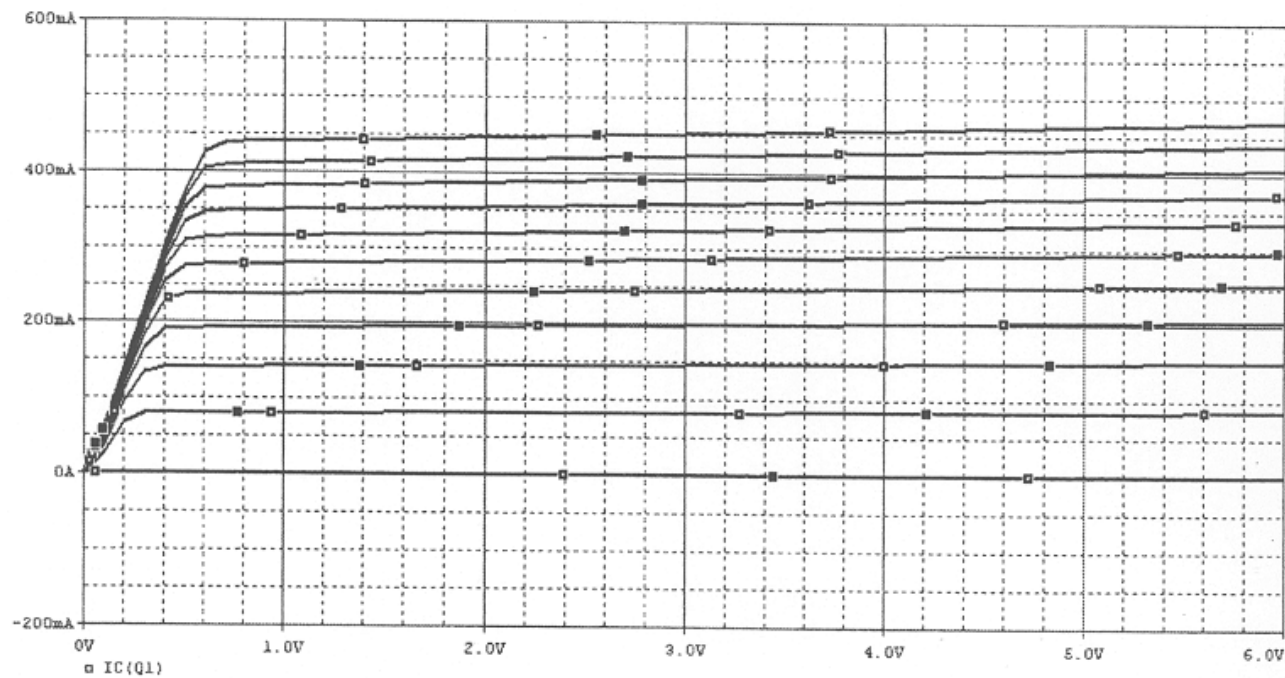
# $V_{CE} - I_C$ Characteristic Simulations

- $V_{CE} - I_C$  characteristic curves with variations of  $I_B$


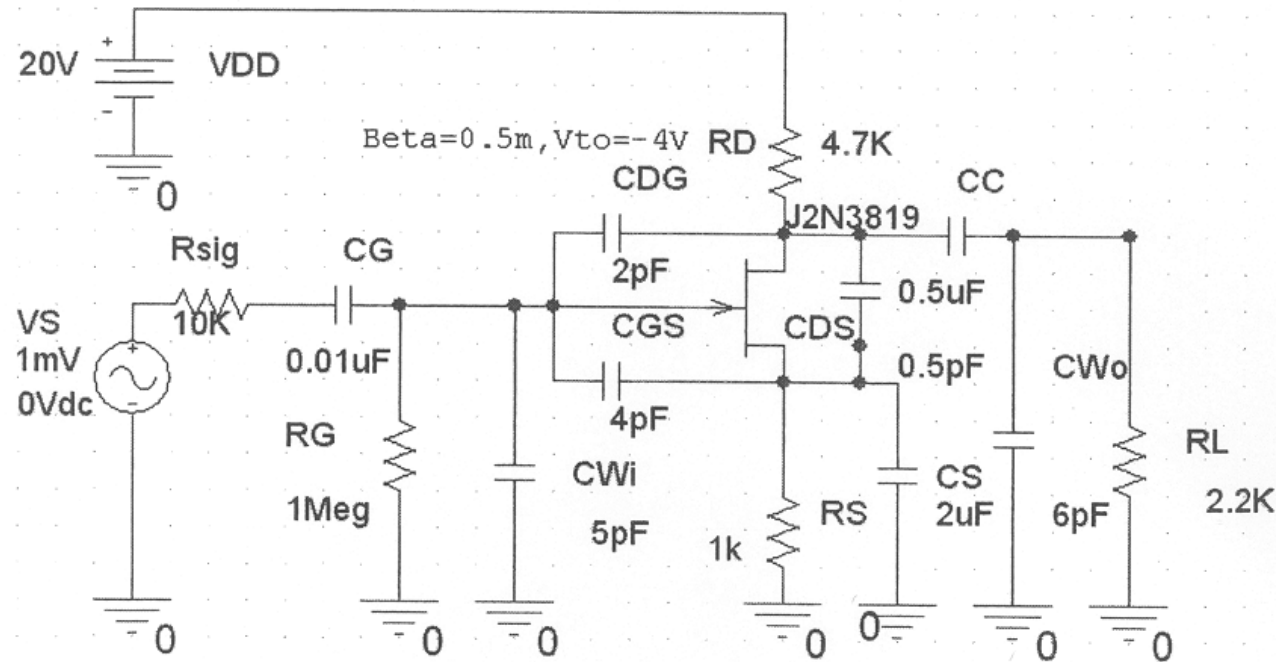
# Amplifier Frequency Response Simulations





✓ Common-source amplifier with parasitic capacitance



# Amplifier Frequency Response Simulations


- Setting dB probe

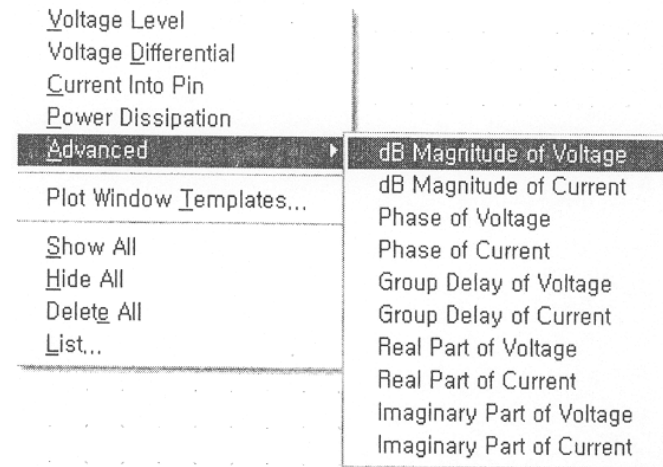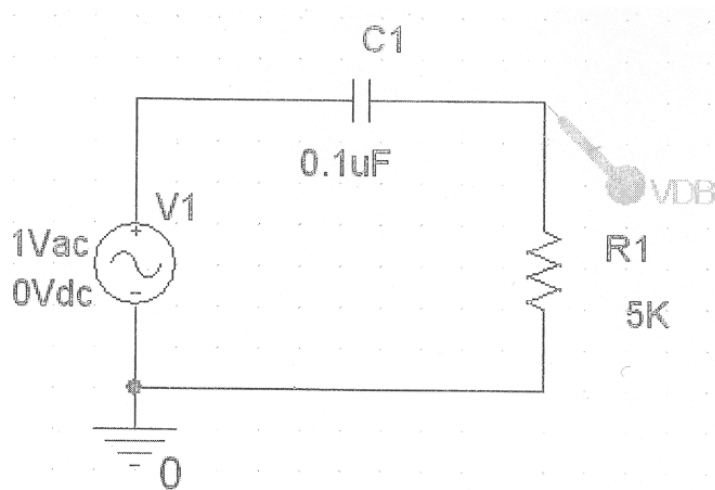




# Amplifier Frequency Response Simulations

- Simulation Settings

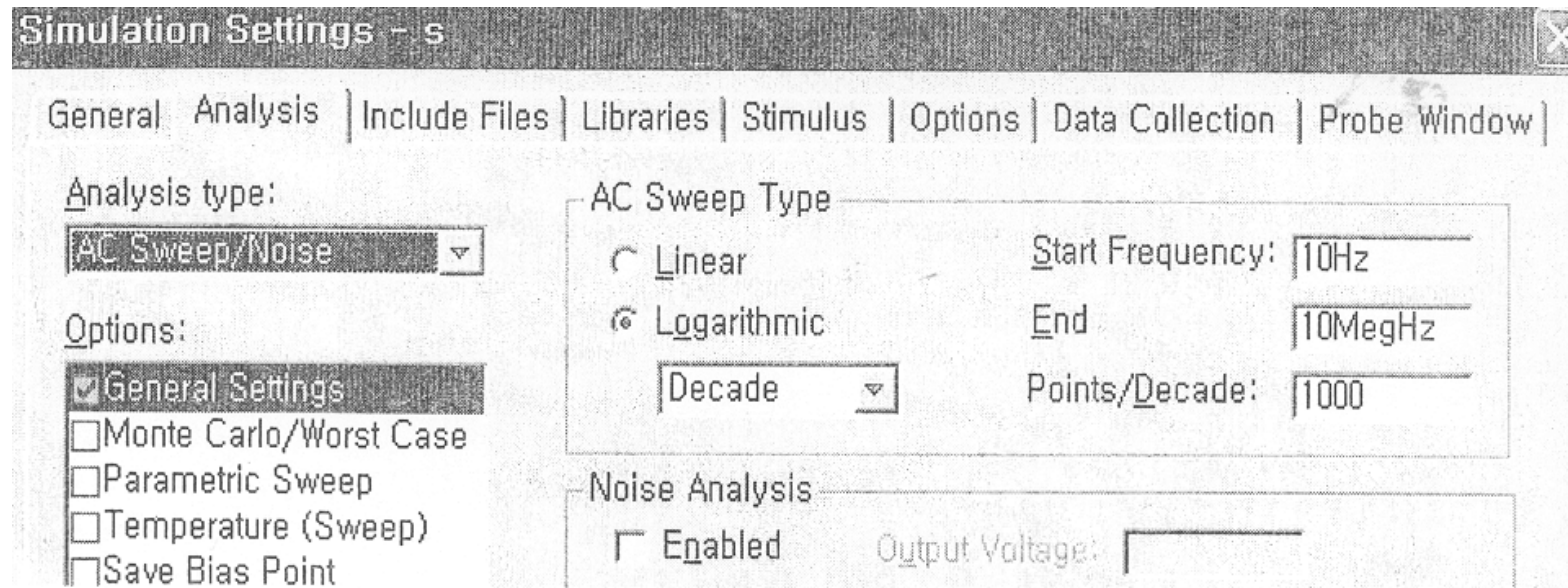

# Amplifier Frequency Response Simulations

- Simulation results (-3dB frequencies)

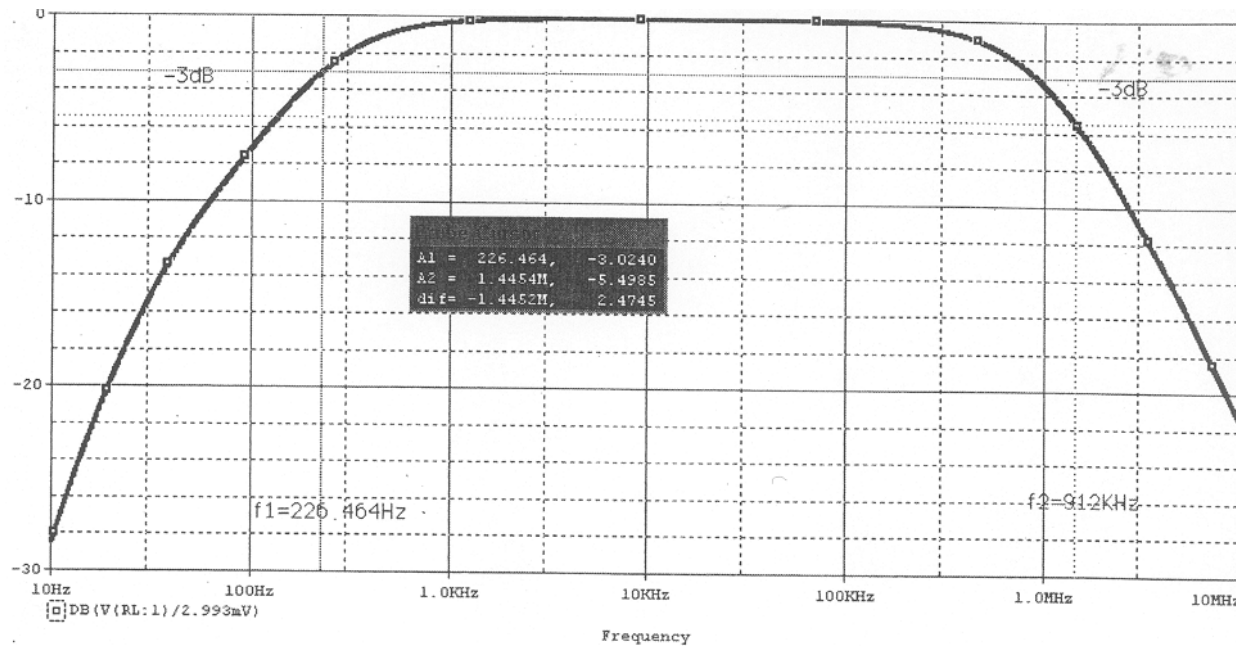

# Pre-report (Lab. 2)

---

- ✓ PSPICE simulations of diodes & rectifiers
- ✓ Submission materials: schematic diagrams and simulation results (waveforms)
- ✓ Make brief!!



# DC biasing

- Thevenin equivalent circuit seen by the base:

$$V_{BB} = \frac{R_2}{R_1 + R_2} V_{CC} \quad R_B = R_1 // R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

- Quiescent emitter current:  $I_{CQ} = \beta I_{BQ}$ ,



$$I_{EQ} = I_{BQ} + I_{CQ} = I_{BQ} + \beta I_{BQ} = (\beta + 1) I_{BQ} = \frac{\beta + 1}{\beta} I_{CQ},$$

- DC bias point:

$$V_{CEQ} = V_{CC} - I_{CQ} R_C - I_{EQ} R_E = V_{CC} - I_{CQ} R_C - \frac{\beta + 1}{\beta} I_{CQ} R_E,$$

$$V_{BEQ} = V_{BB} - I_{BQ} R_B - I_{EQ} R_E = V_{BB} - I_{BQ} R_B - \frac{\beta + 1}{\beta} I_{CQ} R_E.$$

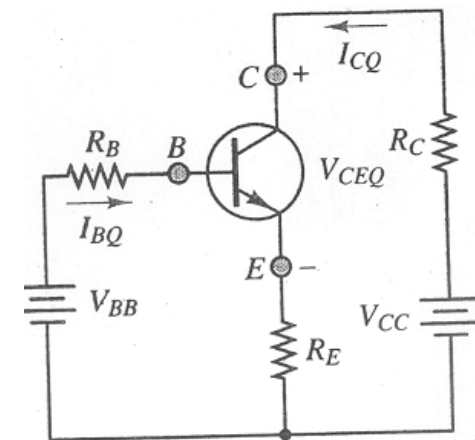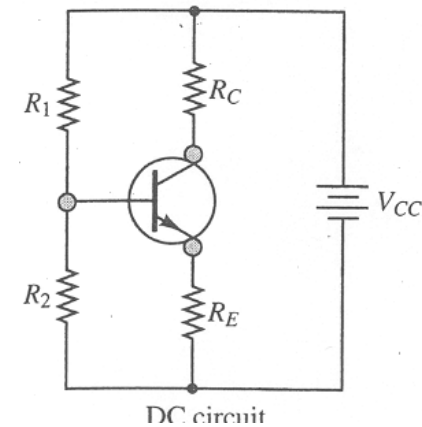- As for amplifiers:  $V_{BEQ} = 0.7V(Si)$ .



# DC biasing

- For the circuit below:  $V_{BB} = \frac{R_2}{R_1 + R_2} = 6.33 \text{ V}$        $R_B = \frac{R_1 R_2}{R_1 + R_2} = 10 \text{ k}\Omega$
- Base-emitter circuit:  $6.33 - 0.7 = I_B R_B + I_E R_E = 10,000 I_B + (101)(200) I_B$ ,  
 $\therefore I_B = \frac{5.63}{30,200} = 186.4 \text{ } \mu\text{A}$ ,  $I_C = \beta I_B = 18.64 \text{ mA}$ .
- $V_{CE} = 15 - 200 I_C - 200 \frac{\beta + 1}{\beta} I_C \cong 7.5 \text{ V}$

