

---


# Lab. 10

# Power Amplifiers



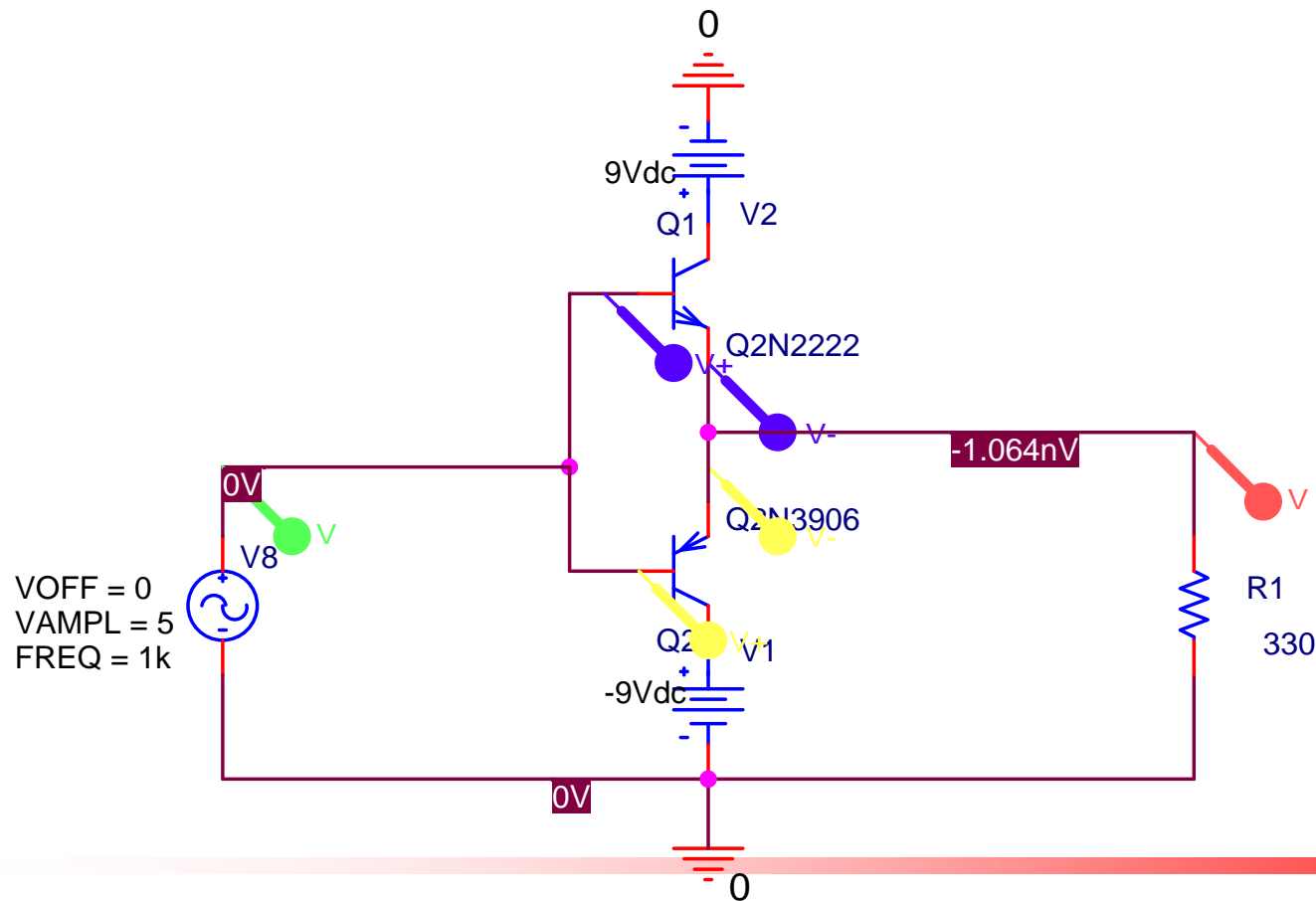
# Class B Push-Pull Power Amp.

- ✓ Class B push-pull PA circuit (pp. 199, Fig. 11-11)


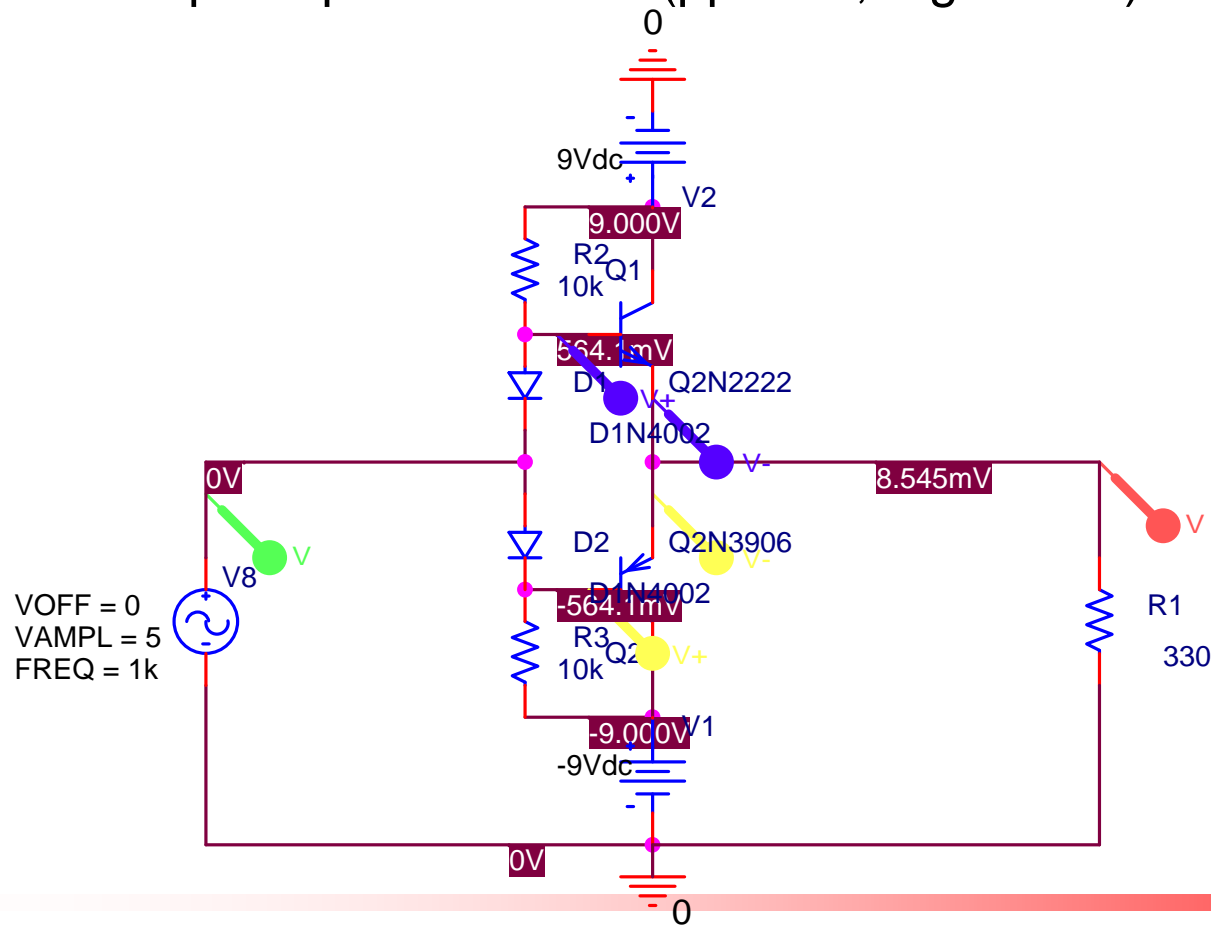
# Class AB Push-Pull PA

- ✓ Class AB push-pull PA circuit (pp. 199, Fig. 11-12)



# Contents of Lab. Report

---

- ✓ Team No.:                      PID:                      Name:
- ✓ Introduction
- ✓ Power Amplifier Results
- ✓ Discussion & Conclusion



# Pre-Report (Lab. 11)

---

- ✓ PSPICE simulations of an Op-amp circuit!
- ✓ Submit the schematic diagrams and the simulation results.
- ✓ No need of introduction and discussion in pre-report.

